

Code: 23EE3201

**I B.Tech - II Semester – Supplementary Examinations
DECEMBER 2025**

**ELECTRICAL CIRCUIT ANALYSIS-I
(ELECTRICAL & ELECTRONICS ENGINEERING)**

Duration: 3 hours

Max. Marks: 70

Note: 1. This question paper contains two Parts A and B.

2. Part-A contains 10 short answer questions. Each Question carries 2 Marks.

3. Part-B contains 5 essay questions with an internal choice from each unit. Each Question carries 10 marks.

4. All parts of Question paper must be answered in one place.

PART – A

1.a)	Illustrate Kirchhoff's current Law with an example.
1.b)	An electric iron is rated 1500W, 230V. Find the current drawn & resistance of the heating element.
1.c)	Define MMF and reluctance.
1.d)	State Faraday's law of Electromagnetic Induction.
1.e)	Define Average and RMS values.
1.f)	An Alternating current is given by $i=28.28\sin (100\pi t)$, find R.M.S value and Average value.
1.g)	Define resonance.
1.h)	Draw the current locus for Series RC circuit with varying Resistance.
1.i)	State millman's theorem.
1.j)	State compensation theorem.

PART – B

			Max. Marks
UNIT-I			
2	a)	Explain in detail about the active elements and passive elements with examples.	5 M
	b)	Derive the equivalent STAR expressions for given DELTA network.	5 M

OR

3	<p>a) Determine the three mesh currents as labeled in the circuit diagram shown below.</p>	6 M
b)	<p>Find the equivalent resistance R_{ab} in the circuit given below?</p>	4 M


UNIT-II

4	<p>a) Derive the expression for the equivalent inductance, when the two mutually coupled inductors are connected in series aiding and series opposition.</p>	5 M
b)	<p>An iron ring of mean circumference 150 cm with area of cross section of 5 cm^2 is wound uniformly with 200 turns of wire. Find the current required to produce a flux of 0.3 mwb in the iron. Assume the relative permeability of iron is 400.</p>	5 M

OR

5	<p>a) Explain about dot convention in mutually coupled circuits</p>	5 M
---	---	-----

	b)	Determine the total inductance, if $L_1=50$ mH, $L_2=200$ mH and $M=100$ mH.	5 M
--	----	--	-----

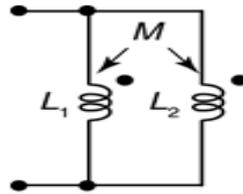


UNIT-III

6	a)	Define Form Factor and crest Factor.	4 M
	b)	Find the form factor and crest factor for the following waveforms i) sinusoidal waveform ii) Half wave rectified sine wave.	6 M

OR

7	a)	Explain the steady state analysis of R-L series circuit and draw the phasor diagram.	4 M
	b)	A series circuit having pure resistance of 50 ohms and an inductance of 0.02 H is connected in parallel with a capacitor of 25 μ F across a 200 V, 50 Hz ac supply as shown in figure below. Calculate the currents I , I_1 , I_2 , total p.f and total power consumed by the circuit.	6 M

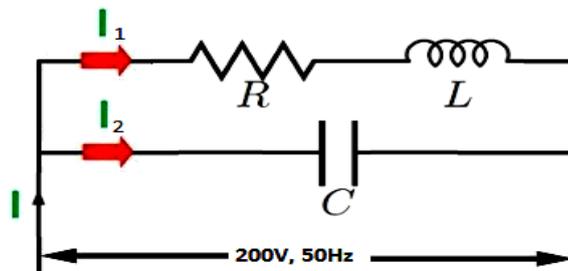


UNIT-IV

8	a)	Derive the equation for resonance frequency of a parallel RLC circuit and bandwidth for a parallel RLC circuit as a function of resonant frequency	5 M
	b)	A series RLC circuit has $R=10$ Ω , $L=0.5$ H and $C=40$ μ F. The applied voltage is 100 V. Find (i) Resonant frequency & Quality factor of a coil (ii) Bandwidth (iii) Upper and Lower half power frequencies.	5 M


OR

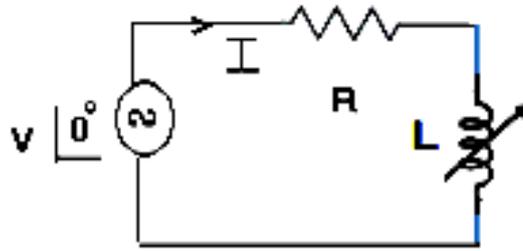- 9 Explain the procedure to draw the locus diagram of R-L series circuit when L is varying. 10 M



UNIT-V

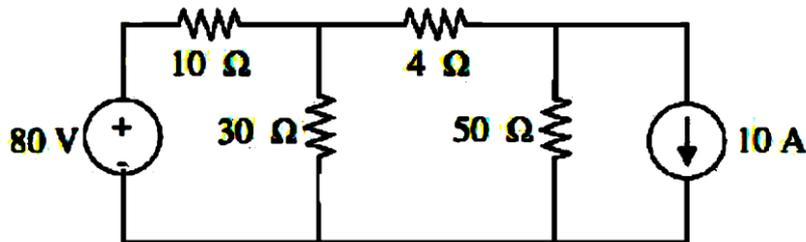- 10 a) State and explain Superposition theorem. 5 M
b) Verify Superposition theorem for 4Ω resistor for the following circuit. 5 M



OR

- 11 a) State and explain Maximum power transfer theorem. 4 M
b) Find the Thevenin's equivalent circuit across A & B terminals. Also draw the Norton's equivalent circuit. 6 M

