

**I B.Tech - II Semester – Regular / Supplementary Examinations  
MAY 2025**

**NETWORK ANALYSIS  
(ELECTRONICS & COMMUNICATION ENGINEERING)**

Duration: 3 hours

Max. Marks: 70

Note: 1. This question paper contains two Parts A and B.

2. Part-A contains 10 short answer questions. Each Question carries 2 Marks.


3. Part-B contains 5 essay questions with an internal choice from each unit. Each Question carries 10 marks.

4. All parts of Question paper must be answered in one place.

BL – Blooms Level



CO – Course Outcome

**PART – A**

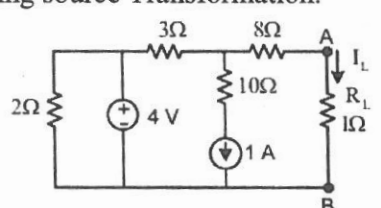		BL	CO
1.a)	Explain dependent sources with an example.	L2	CO1
b)	Explain Independent sources with an example.	L2	CO1
c)	Draw the phasor diagram of a series RC circuit.	L2	CO3
d)	State Thevenin's theorem.	L2	CO2
e)	Find $I_L$ using source Transformation.	L2	CO2
			
f)	In a series RLC circuit, $R=60k\Omega$ , $L=20mH$ , $C=245\mu F$ . Find the resonant frequency.	L2	CO4
g)	What are the conditions to be fulfilled for Symmetry of a two-port network?	L2	CO5
h)	Give the comparison between Series and Parallel resonance.	L2	CO4

i)	State any two properties of Laplace transform.	L1	CO3
j)	Define Y-parameters and g-parameters.	L1	CO5

**PART – B**

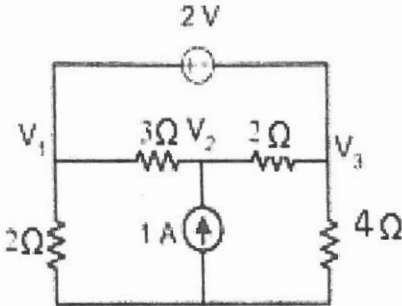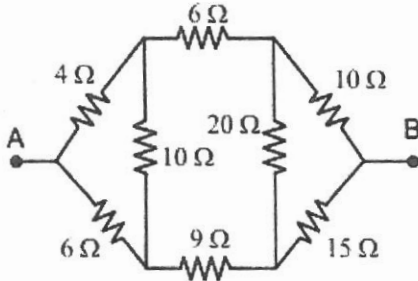			BL	CO	Max. Marks
<b>UNIT-I</b>					
2	a)	Determine all the node voltages using nodal analysis for the network shown in the fig.	L3	CO2	5 M
					
	b)	Determine the equivalent resistance between terminals A and B for the circuit shown in fig.	L3	CO1	5 M
					
<b>OR</b>					

3	a)	Determine all the node voltages using nodal analysis.	L3	CO2	5 M
	b)	Explain Super node concept with an example.	L2	CO2	5 M

### UNIT-II

4		Obtain the Thevenin's equivalent network for the circuit shown in Figure.	L3	CO2	10 M

OR

5	a)	Find the value of $Z_L$ for which maximum power is transfer occurs in the circuit shown in Figure.	L3	CO2	5 M




	b)	For the circuit shown in Figure, using superposition theorem find the current flowing through a load resistance $R_L = 10\Omega$ .	L3	CO2	5 M



### UNIT-III

6	a)	Derive the expression for resonant frequency of a series RLC Circuit.	L3	CO4	5 M
	b)	Two coils with a coefficient of coupling of 0.4 between them are connected in series so as to magnetize in (a) same direction and b) opposite direction. The total inductance in the same direction is 1.8 H and in the opposite direction is 0.8H. Find the self-inductance of the coils.	L3	CO4	5 M

OR

7		An RLC series circuit with a resistance of 100, inductance of 0.2H and a capacitance of 40μF is supplied with a 100V supply at Variable frequency. Find the following parameters for the series resonant circuit. (i) Frequency of which resonance takes place (ii) current (iii) power (iv) power factor (v) Quality factor (g) half-power frequencies.	L3	CO4	10 M
---	--	--	----	-----	------

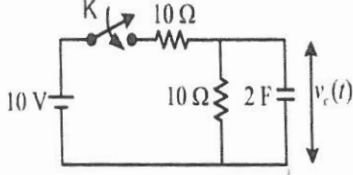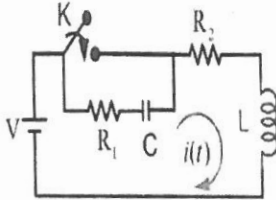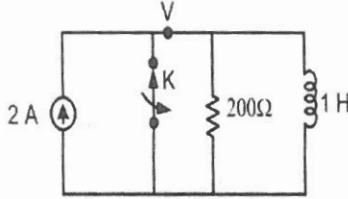UNIT-IV				
8	a)	Explain the procedure for obtaining the transient response using Laplace transform.	L2	CO3 5 M
	b)	The switch in the network shown in Figure is closed at $t = 0$ . Determine the voltage across the capacitor. 	L4	CO3 5 M
OR				
9	a)	Consider an RLC series circuit as shown figure. Let us assume that the capacitor and inductor are initially uncharged, that is, at $t=0$ , there is no charge on L or C. Develop an expression for current in the circuit when switch K is closed at $t = 0$ . 	L3	CO3 5 M
	b)	For the circuit shown in figure, Analyse the circuit after switch is closed at $t=0$ and find the transient current for $t>0$ . 	L4	CO3 5 M

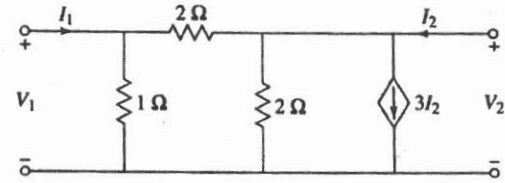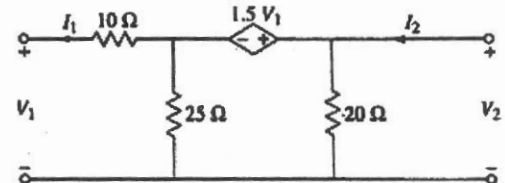UNIT-V				
10	a)	For the network shown in Figure, Find Y parameters. 	L3	CO5 5 M
	b)	Express h parameters in terms of ABCD parameters.	L3	CO5 5 M
OR				
11	For the network shown in figure Find Z and T parameters. 		L3	CO5 10 M

**I B.Tech - II Semester — Regular / Supplementary Examinations**

**MAY' 2025**

**NETWORK ANALYSIS (23EC3201)**

**(ELECTRONICS & COMMUNICATION ENGINEERING)**

**PART — A**

- 1.a) Explain dependent sources with an example.

Definition with one example ----- 2Marks

- b) Explain Independent sources with an example.

Definition with one example ----- 2Marks


- c) Draw the phasor diagram of a series RC circuit.

Phasor diagram ----- 2Marks

- d) State Thevenin's theorem.

Statement for Thevenin's theorem ----- 2Marks

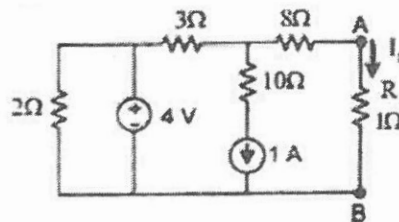- e) Find  $I_L$  using source Transformation.



Calculation of  $I_L$ ----- 2Marks

- f) In a series RLC circuit,  $R=60K\Omega$ ,  $L = 20mH$ ,  $C=245\mu F$ . Find the resonant frequency.

Formula ----- 1Mark

Calculation ----- 1Mark

- g) What are the conditions to be fulfilled for Symmetry of a two- port network?

Condition for Symmetry of a two- port network ----- 2Marks

- h) Give the comparison between Series and Parallel resonance.

Any Two comparisons between Series and Parallel resonance ----- 2Marks

- i) State any two properties of Laplace transform.

Any two properties of Laplace transform ----- 2Marks

- j) Define Y-parameters and g-parameters.


Y-parameters ----- 1 Mark

g-parameters ----- 1 Mark

## PART — B

### UNIT-I

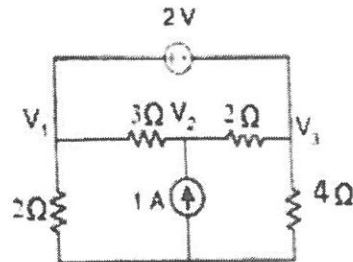
2. a) Determine all the node voltages using nodal analysis for the network shown in the fig.



Node Equations -----3 Marks

Solving Equations -----2 Marks

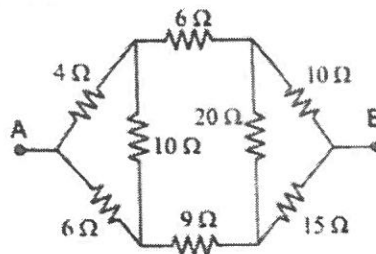
- b) Determine the equivalent resistance between terminals A and B for the circuit shown in fig.



Delta to star conversion ----- 3 Marks

Solving the network ----- 2 Marks

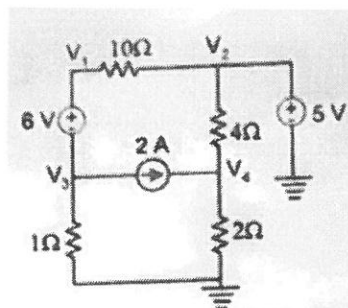3. a) Determine all the node voltages using nodal analysis.



Node Equations -----3 Marks

Solving Equations -----2 Marks


b) Explain Super node concept with an example.

Super node concept -----2 Marks

Example -----3 Marks

## UNIT-II

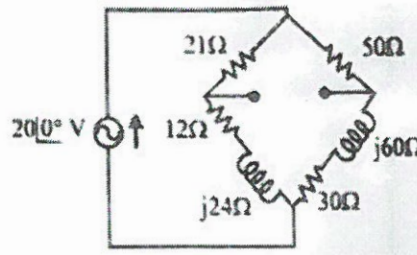4. Obtain the Thevenin's equivalent network for the circuit shown in Figure.




Calculation of  $V_{Th}$  -----4 Marks

Calculation of  $Z_{Th}$  -----4 Marks

Thevenin's Equivalent Network -----2 Marks

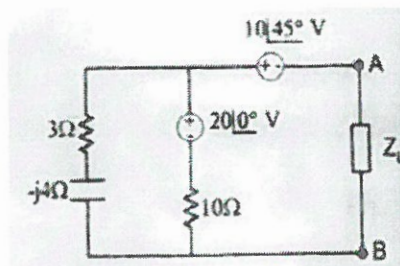5. a) Find the value of  $Z_L$  for which maximum power is transfer occurs in the circuit shown in Figure.




Calculation of  $Z_{Th}$ : ----- 4 Marks

Condition for Maximum Power Transfer ----- 1Mark

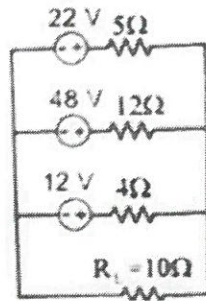b) For the circuit Shown in Figure, using superposition theorem find the current flowing through a load resistance  $R_L = 10\Omega$ .





Each Case ----- 1.5 Marks  $= 3 \times 1.5 = 4.5 \text{ Marks}$

Calculation of  $I_L$  ----- 0.5 Marks

6. a) Derive the expression for resonant frequency of a series RLC Circuit.

Series RLC Circuit Diagram ----- 2Marks

Derivation for resonant frequency ----- 3Marks

- b) Two coils with a coefficient of coupling of 0.4 between them are connected in series so as to magnetize in (a) same direction and b) opposite direction. The total inductance in the same direction is 1.8 H and in the opposite direction is 0.8H. Find the self-inductance of the coils.

Formulas ----- 3Marks

Calculations ----- 2Marks

7. An RLC series circuit with a resistance of 100, inductance of 0.2H and a capacitance of  $40\mu\text{F}$  is supplied with a 100V supply at Variable frequency. Find the following parameters for the series resonant circuit. (i) Frequency of which resonance takes place (ii) current (iii) power (iv) power factor (v) Quality factor (g) half-power frequencies.

Formulas ----- 6Marks


Calculations ----- 4Marks

8. a) Explain the procedure for obtaining the transient response using Laplace Transform.

Procedure ----- 5Marks

- b) The switch in the network shown in figure is closed at  $t=0$ . Determine the voltage across


the capacitor.

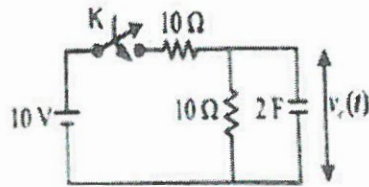

Mesh equations & Laplace transform ----- 3Marks

Calculation of voltage across the capacitor ----- 2Marks

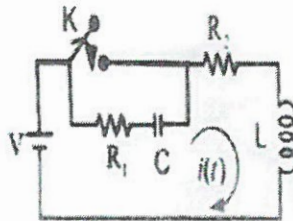9. a) Consider an RLC series circuit as shown figure. Let us assume that the capacitor and inductor are initially uncharged, that is, at  $t=0$ , there is no charge on L or C. Develop an expression for current in the circuit when switch K is closed at  $t = 0$ .




Circuit Analysis at  $t=0^-$  ----- 1Mark

Circuit Analysis at  $t=0^+$  ----- 2Marks

Circuit Analysis at  $t > 0$  ----- 2Marks

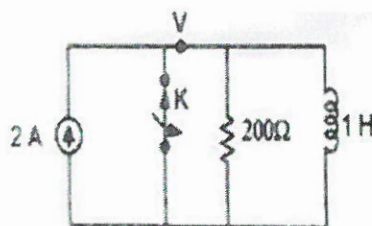
- b) For the circuit shown in figure, Analyse the circuit after switch is closed at  $t=0$  and find the transient current for  $t > 0$ .



Calculation of transient current----- 5Marks

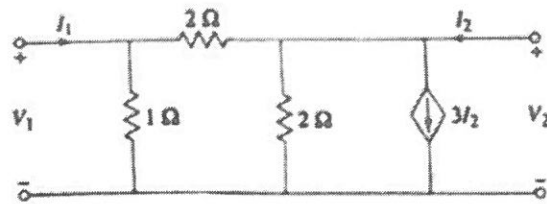10. a) For the network shown in Figure, Find Y parameters.





Nodal Equations ----- 3Marks


Calculation of Y parameters ----- 2Marks

b) Express h parameters in terms of ABCD parameters.

h parameters & ABCD parameters equations ----- 2Marks

h parameters in terms of ABCD parameters ----- 3Marks

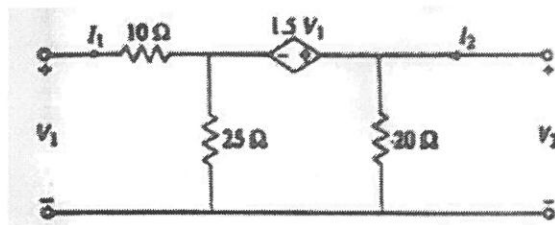11. For the network shown in figure Find Z and T parameters.



Z and T parameters equations ----- 2Marks

Calculation of Z parameters ----- 4Marks

Calculation of T parameters ----- 4Marks

I B.Tech - II Semester — Regular / Supplementary Examinations

MAY' 2025


NETWORK ANALYSIS (23EC3201)

(ELECTRONICS & COMMUNICATION ENGINEERING)

PART — A

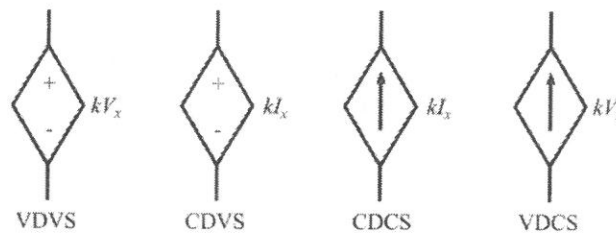1.a) Explain dependent sources with an example.

If the voltage or current of a source **depends** upon some other voltage or current, it is called as **dependent or controlled source**.



b) Explain Independent sources with an example.

If the voltage or current of a source **does not depend** upon some other voltage or current, it is called as **independent source**.

Independent Voltage Source

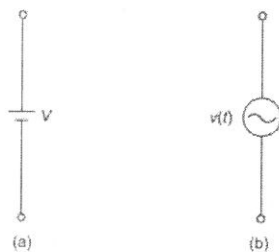


Fig. 1.1 Independent voltage source

Independent Current Source


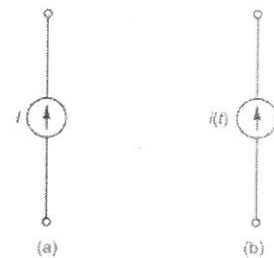


Fig. 1.2 Independent current source

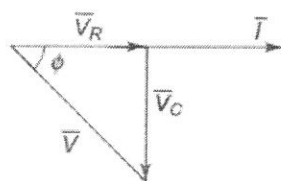c) Draw the phasor diagram of a series RC circuit.



The phasor diagram for RC circuit is shown in Fig below.

Where  $V$  is the applied voltage.

$V_R$  is the Potential difference across the resistor.


$V_C$  is the Potential difference across the capacitor.

**d) State Thevenin's theorem.**


Thevenin's theorem states that "Any two terminal linear network having a number of voltage current sources and resistances can be replaced by a equivalent circuit consisting of a single voltage source in series with a resistance."

where the value of the voltage source is equal to the open-circuit voltage across the two terminals of the network, and resistance is equal to the equivalent resistance measured between the terminals with all the energy sources are replaced by their internal resistances.


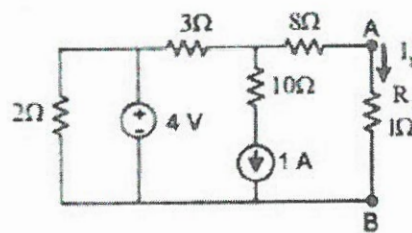
**e) Find  $I_L$  using source Transformation.**



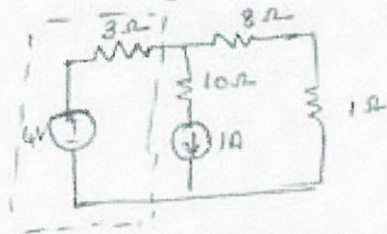*e* As the voltage across  $2\Omega$  is also  $4V$  neglecting  $2\Omega$



Applying source transformation

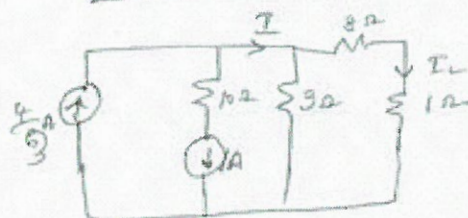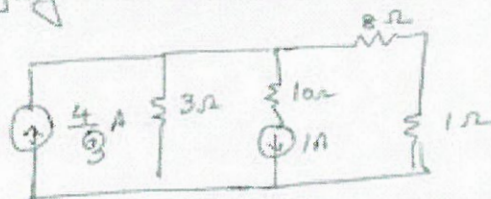

$$I = \frac{4}{3} - 1 = \frac{1}{3} A$$

Applying current Division

$$I_L = \frac{1}{3} \times \frac{3}{3+9}$$

$$= \frac{1}{12} = 83.33 \text{ mA}$$

$I_L = 83.33 \text{ mA}$

f) In a series RLC circuit,  $R=60\text{K}\Omega$ ,  $L = 20\text{mH}$ ,  $C=245\mu\text{F}$ . Find the resonant frequency.

For a series RLC circuit resonant frequency  $f_0$  is given by  $f_0 = \frac{1}{2\pi\sqrt{LC}}$

$$L=20\text{mH}=20\times 10^{-3}\text{H}$$

$$C=245\mu\text{F}=245\times 10^{-6}\text{F}$$

$$f_0 = \frac{1}{2\pi\sqrt{(20 \times 10^{-3})(245 \times 10^{-6})}}$$

$$f_0=71.9\text{Hz}$$

g) What are the conditions to be fulfilled for Symmetry of a two- port network?

For a network to be symmetrical, the voltage-to-current ratio at one port should be the same as the voltage to- current ratio at the other port with one of the ports open-circuited.

h) Give the comparison between Series and Parallel resonance.

Comparison between Series and Parallel resonance:

Parameter	Series Circuit	Parallel Circuit
Current at resonance	$I = \frac{V}{R}$ and is maximum	$I = \frac{VCR}{L}$ and is minimum
Impedance at resonance	$Z = R$ and is minimum	$Z = \frac{L}{CR}$ and is maximum
Power factor at resonance	Unity	Unity
Resonant frequency	$f_0 = \frac{1}{2\pi\sqrt{LC}}$	$f_0 = \frac{1}{2\pi\sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}}$
Q-factor	$Q = \frac{2\pi f_0 L}{R}$	$Q = \frac{2\pi f_0 L}{R}$
It magnifies	Voltage across $L$ and $C$	Current through $L$ and $C$

i) State any two properties of Laplace transform.

**Properties of Laplace Transform:**

**1. Linearity:**

If  $L\{f_1(t)\} = F_1(s)$  and  $L\{f_2(t)\} = F_2(s)$  then  $L\{af_1(t) + bf_2(t)\} = aF_1(s) + bF_2(s)$   
where  $a$  and  $b$  are constants.

**2. Time Scaling:**

If  $L\{f(t)\} = F(s)$  then  $L\{f(at)\} = \frac{1}{a}F\left(\frac{s}{a}\right)$

j) Define Y-parameters and g-parameters.

**Y-parameters:**

The Y parameters of a two-port network may be defined by expressing the two-port currents  $I_1$  and  $I_2$  in terms of the two-port voltages  $V_1$  and  $V_2$ .

$$I_1 = Y_{11} V_1 + Y_{12} V_2$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2$$

**g-parameters:**

The g parameters of a two-port network are defined by expressing the current of the input port  $I_1$  and voltage of the output port  $V_2$  in terms of the voltage of the input port  $V_1$  and the current of the output port  $I_2$ .


$$I_1 = g_{11} V_1 + g_{12} I_2$$

$$V_2 = g_{21} V_1 + g_{22} I_2$$

## PART — B

### UNIT-I

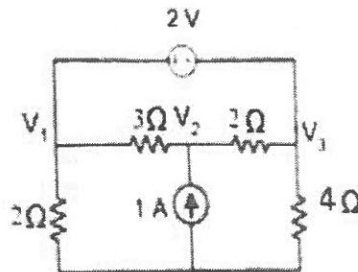2. a) Determine all the node voltages using nodal analysis for the network shown in the fig.



In the above figure as 2V voltage source is connected between Nodes 1 & 3, Node 1 & 3 will form a Super Node.

Applying KVL to super node:

$$V_1 - V_3 = 2V \quad \text{----- 1}$$

Applying KCL to super node:

$$\frac{V_1}{2} + \frac{V_1 - V_2}{3} + \frac{V_3 - V_2}{2} + \frac{V_3}{4} = 0 \quad \text{-----2}$$


Applying KCL to  $V_2$ :

$$\frac{V_2 - V_1}{3} + \frac{V_2 - V_3}{2} - 1 = 0 \quad \text{-----3}$$

Solving Equ's 1, 2 & 3


$$V_1 = 2V, V_2 = 2V, V_3 = 0V$$

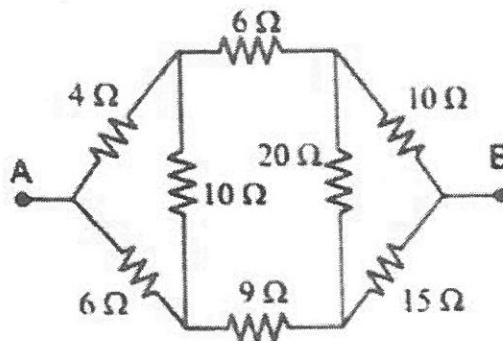- b) Determine the equivalent resistance between terminals A and B for the circuit shown in fig.






2. b

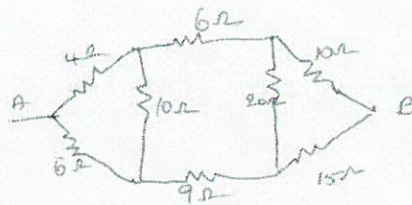

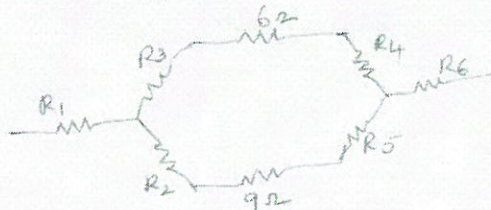Solu: Converting 2 delta's into equivalent star network.



$$R_1 = \frac{4 \times 6}{4 + 6 + 10} = \frac{24}{20} = 1.2 \Omega$$



$$R_4 = \frac{20 \times 10}{20 + 10 + 15} = \frac{200}{45} = 4.44 \Omega$$

$$R_2 = \frac{6 \times 10}{4 + 6 + 10} = \frac{60}{20} = 3 \Omega$$



$$R_5 = \frac{15 \times 20}{15 + 20 + 10} = \frac{300}{45} = 6.66 \Omega$$

$$R_3 = \frac{4 \times 10}{4 + 6 + 10} = \frac{40}{20} = 2 \Omega$$
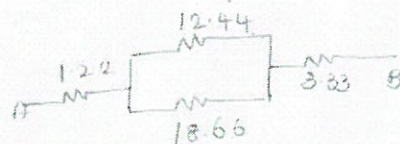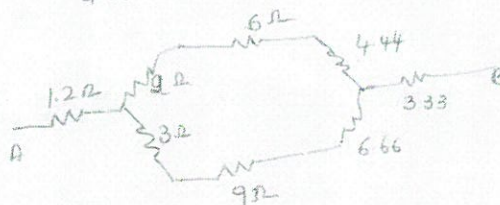
$$R_6 = \frac{10 \times 15}{15 + 20 + 10} = \frac{150}{45} = 3.33 \Omega$$




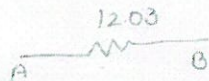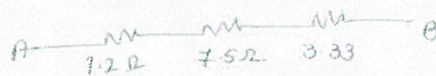
$$12.44 \parallel 18.66 = \frac{12.44 \times 18.66}{12.44 + 18.66} = \frac{232.13}{31.1} = 7.5 \Omega$$



$$R_{AB} = 12.03 \Omega$$

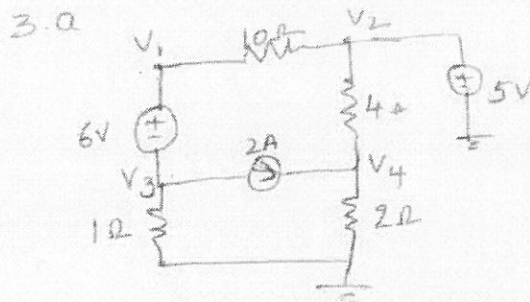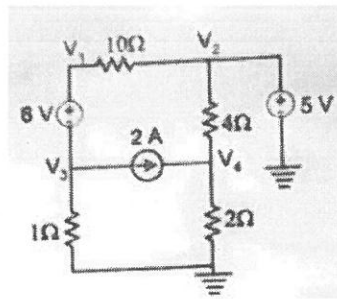3. a) Determine all the node voltages using nodal analysis.



From the diagram  $V_2 = 5V$  — (1)

$V_1$  &  $V_3$  are forming supernode

$$V_1 - V_3 = 6V \quad \text{--- (2)}$$

Applying KCL to supernode

$$\frac{V_3}{1} + 2 + \frac{V_1 - V_2}{10} = 0 \quad \text{--- (3)}$$

Applying KCL to node  $V_4$

$$\frac{V_4}{2} + \frac{V_4 - V_2}{4} - 2 = 0 \quad \text{--- (4)}$$

### Solving Equations 1, 2, 3 & 4

$$V_1 = 4V$$

$$V_2 = 5V$$

$$V_3 = -1.91V$$


$$V_4 = 4.33V$$

### b) Explain Super node concept with an example.


#### Supernode Analysis:

Nodes that are connected to each other by voltage sources, but not to the reference node by a path of voltage sources, form a super node. A super node requires one node voltage equation, that is, a KVL equation. The remaining node voltage equations are KCL equations.

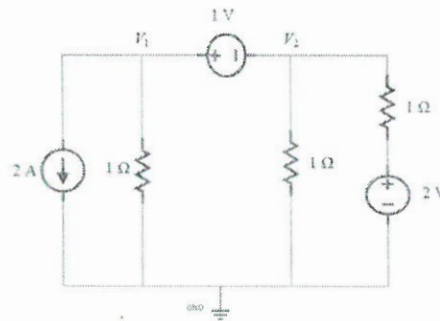**Example:** To find the nodal voltages  $V_1$  and  $V_2$  in the network shown in Fig.



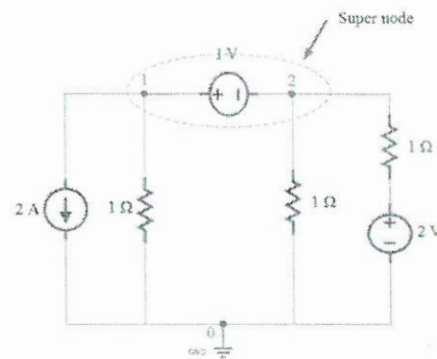In the above figure as 1V voltage source is connected between Nodes 1 & 2, Node 1 & 2 will form a Super Node.



Applying KVL to super node:

$$V_1 - V_2 = 1V \quad \text{----- 1}$$

Applying KCL to super node:

$$2 + \frac{(V_1 - 0)}{1} + \frac{(V_2 - 0)}{1} + \frac{(V_2 - 2)}{1} = 0 \quad \text{----- } 2$$


Solving Eq's 1 & 2

$$V_1 = 2/3 = 1.5V$$


$$V_2 = -1/3 = 0.33V$$

## UNIT-II

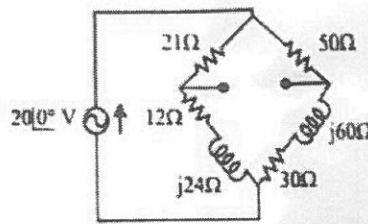4. Obtain the Thevenin's equivalent network for the circuit shown in Figure.



Calculation of  $V_{Th}$ :

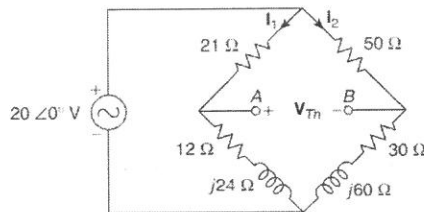


$$I_1 = \frac{20\angle 0^\circ}{21 + 12 + j24} = 0.49\angle -36.02^\circ \text{ A}$$

$$I_2 = \frac{20\angle 0^\circ}{80 + j60} = 0.2\angle -36.86^\circ \text{ A}$$


$$\begin{aligned} V_{Th} &= (12 + j24) I_1 - (30 + j60) I_2 \\ &= (26.83 \angle 63.43^\circ) (0.49 \angle -36.02^\circ) - (67.08 \angle 63.43^\circ) (0.2 \angle -36.86^\circ) \\ &= 0.33 \angle 171.12^\circ \text{ V} \end{aligned}$$

Calculation of  $Z_{Th}$ :

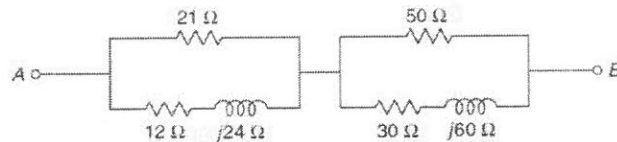


$$Z_{Th} = \frac{21(12 + j24)}{33 + j24} + \frac{50(30 + j60)}{80 + j60} = 47.4 \angle 26.8^\circ \Omega$$

### Thevenin's Equivalent Network:

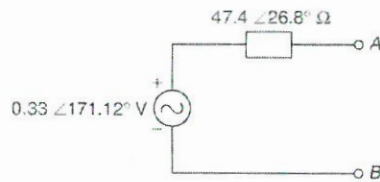

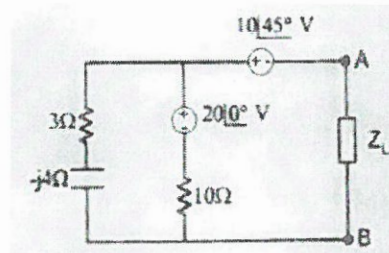5. a) Find the value of  $Z_L$  for which maximum power is transfer occurs in the circuit shown in Figure.



The Thevenin's impedance is:

$$Z_{th} = ((3 - j4) || (10))$$

$$Z_{th} = \frac{((3 - j4)(10))}{((3 - j4) + (10))} = \frac{30 - j40}{13 - j4}$$

$$Z_{th} = \frac{30 - j40}{13 - j4} \cdot \frac{13 + j4}{13 + j4}$$


$$Z_{th} = \frac{550 - j400}{185}$$

$$Z_{th} = 2.97 - j2.16$$


Condition for Maximum Power Transfer is  $Z_L = Z_{th}^*$

$$Z_{th} = Z_{th}^* = 2.97 + j2.16$$


- b) For the circuit Shown in Figure, using superposition theorem find the current flowing through a load resistance  $R_L = 10\Omega$ .

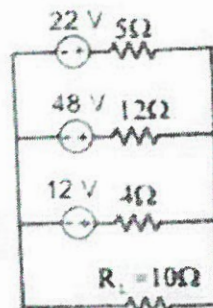



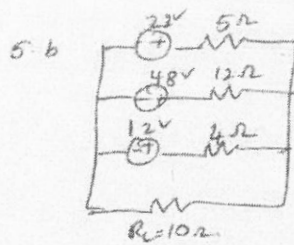

Case I : 22V source is active

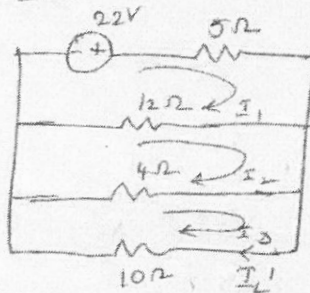

Mesh 1

$$17I_1 - 12I_2 = 22$$

Mesh 2

$$-12I_1 + 16I_2 - 4I_3 = 0$$

Mesh 3

$$-4I_2 + 14I_3 = 0$$

Solving above eq's


$$I_1 = 3 \text{ A}$$

$$I_2 = 2.43 \text{ A}$$

$$I_3 = 0.69 \text{ A}$$

$$I_{L'} = I_3 = 0.69 \text{ A}$$

Case II : 48V source is active

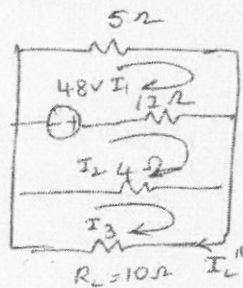

Mesh 1

$$17I_1 - 12I_2 = -48$$

Mesh 2

$$-12I_1 + 16I_2 - 4I_3 = 48$$

Mesh 3

$$-4I_2 + 14I_3 = 0$$

Solving above eq's

$$I_1 = -1.26 \text{ A}$$


$$I_2 = 2.2 \text{ A}$$

$$I_3 = 0.63 \text{ A}$$

$$I_{L''} = I_3 = 0.63 \text{ A}$$



Case iii : 12V source is active

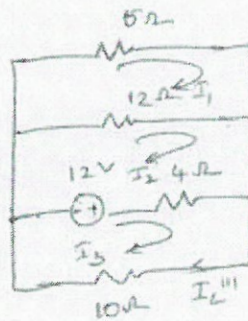

Mesh 1

$$17I_1 + 12I_2 = 0$$

Mesh 2

$$-12I_1 + 16I_2 - 4I_3 = -12$$

Mesh 3

$$-4I_2 + 14I_3 = 12$$

Solving above eq's

$$I_1 = -0.95 \text{ A}$$

$$I_2 = -1.34 \text{ A}$$

$$I_3 = 0.47 \text{ A}$$

$$I_L''' = I_3 = 0.47 \text{ A}$$

$$I_L = I_L' + I_L'' + I_L''' = 0.69 + 0.63 + 0.47$$


$$I_L = 1.79 \text{ A}$$

6. a) Derive the expression for resonant frequency of a series RLC Circuit.

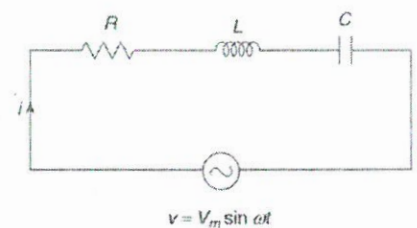**Series Resonance:**

**Resonance:** A circuit containing reactance is said to be in resonance **if the voltage across the circuit is in phase with the current through it**. At resonance, the circuit behaves as a pure resistor and the net reactance is zero.

➤ Consider the **series RLC circuit** shown in Fig



$$\mathbf{Z} = R + jX_L - jX_C = R + j(X_L - X_C)$$

At resonance, the circuit is purely resistive.

$$X_L - X_C = 0$$

$$X_L = X_C$$

$$\omega_0 L = \frac{1}{\omega_0 C}$$

$$\omega_0^2 = \frac{1}{LC}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

where  $f_0$  is called the **resonant frequency** of the circuit.

- b) Two coils with a coefficient of coupling of 0.4 between them are connected in series so as to magnetize in (a) same direction and b) opposite direction. The total inductance in the same direction is 1.8 H and in the opposite direction is 0.8H. Find the self-inductance of the coils.

The coefficient of coupling between the coils is  $k=0.4$ .

The total inductance when the coils are connected in series to magnetize in the same direction is

$$\mathbf{L_{same} = L_1 + L_2 + 2M = 1.8H \quad \text{----- 1}}$$

The total inductance when the coils are connected in series to magnetize in the opposite direction is

$$\mathbf{L_{opposite} = L_1 + L_2 - 2M = 0.8H \quad \text{-----2}}$$

Solving Eq's 1 & 2

$$\mathbf{L_1 + L_2 = 1.3 \quad \text{----- 3}}$$

Substituting Eq 3 in Eq 1

$$\mathbf{L_{same} = L_1 + L_2 + 2M = 1.8H}$$

$$\mathbf{1.3 + 2M = 1.8H}$$

$$2M = 1.8 - 1.3$$

$$2M = 0.5$$

$$M = 0.25$$

The mutual inductance is

$$M = k\sqrt{L_1 L_2}$$

$$\sqrt{L_1 L_2} = \frac{M}{k} = \frac{0.25}{0.4} = 0.625$$

$$L_1 L_2 = 0.39 \text{ ----- } 4$$

Solving Eq's 3 & 4

$$L_1 = 0.052, L_2 = 1.28$$

**7. An RLC series circuit with a resistance of 100, inductance of 0.2H and a capacitance of 40μF is supplied with a 100V supply at Variable frequency. Find the following parameters for the series resonant circuit. (i) Frequency of which resonance takes place (ii) current (iii) power (iv) power factor (v) Quality factor (g) half-power frequencies.**

**Solution:**

$$R = 100\Omega, L = 0.2 \text{ H}, C = 40\mu\text{F}, V = 100 \text{ V}$$

(a) Resonant frequency:

$$f_0 = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{0.2 \times 40 \times 10^{-6}}} = 56.3 \text{ Hz}$$

(b) Current:

$$I = \frac{V}{R} = \frac{100}{100} = 1\text{A}$$

(c) Power:

$$P_0 = I_0^2 R = 1^2 \times 100 = 100\text{W}$$

(d) Power factor:

$$\text{pf} = 1$$

(e) Voltage across R, L, C:

$$V_R = R \times I = 100 \times 1 = 100\text{V}$$

$$V_C = X_C I = \frac{1}{2\pi f C} \times I = \frac{1}{2\pi \times 56.3 \times 40 \times 10^{-6}} \times 1 = 70.7\text{V}$$

$$V_L = X_L I = 2\pi f L \times I = 2\pi \times 56.3 \times 0.2 \times 1 = 70.7\text{V}$$

(f) Quality factor:

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{1}{100} \sqrt{\frac{0.2}{40 \times 10^{-6}}} = 0.707$$

(g) Half-power points:

$$f_1 = f_0 - \frac{R}{4\pi L} = 56.3 - \frac{100}{4\pi \times 0.2} = 56.3 - 39.8 = 16.51 \text{ Hz}$$

$$f_2 = f_0 + \frac{R}{4\pi L} = 56.3 + \frac{100}{4\pi \times 0.2} = 56.3 + 39.8 = 96 \text{ Hz}$$

8. a) Explain the procedure for obtaining the transient response using Laplace Transform.

**1. Define the Circuit and Initial Conditions**

- Identify all elements: resistors (R), capacitors (C), inductors (L), voltage and current sources.
- Note the **initial conditions**.

**2. Transform the Circuit to s-Domain**

- Replace energy-storing elements (L, C) with their **Laplace equivalents**.

Time-Domain Element	s-Domain Equivalent
Resistor R	R
Inductor L	sL
Capacitor C	1/sC

- Apply **initial conditions** as voltage or current sources in the transformed circuit.

**3. Apply Circuit Analysis in s-Domain**

- Use **Nodal or Mesh Analysis** to write algebraic equations.


**4. Solve for the Laplace-Domain Variable**

- Simplify the algebraic equation to obtain the expression for the Laplace-domain response (e.g., current or voltage).


**5. Apply Inverse Laplace Transform**

- Use standard Laplace Transform tables or partial fraction decomposition to invert  $I(s)$  or  $V(s)$  back into the time domain **transient response**  $i(t)$  or  $v(t)$ .

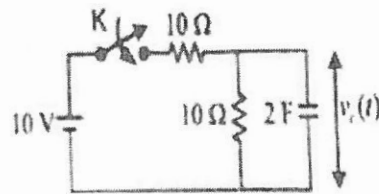
- b) The switch in the network shown in figure is closed at  $t=0$ . Determine the voltage across the capacitor.



8 b. Switch is closed at  $t=0$

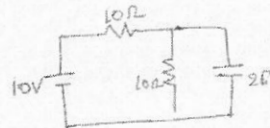

Using Laplace transformation

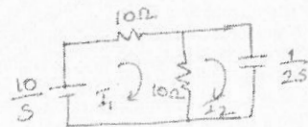

Applying KVL to mesh ①

$$20I_1(s) - 10I_2(s) = \frac{10}{s} \quad \text{--- (1)}$$

$$2I_1(s) - I_2(s) = \frac{1}{s} \quad \text{--- (1)}$$

Applying KVL to mesh ②

$$-10I_1(s) + 10I_2(s) + \frac{1}{2s}I_2(s) = 0$$

$$-10I_1(s) + \left[10 + \frac{1}{2s}\right]I_2(s) = 0$$

$$-10I_1(s) + \left[\frac{20s+1}{2s}\right]I_2(s) = 0$$

$$I_1(s) = \frac{\left[\frac{20s+1}{2s}\right]I_2(s)}{10}$$

$$I_1(s) = \left[\frac{20s+1}{20s}\right]I_2(s) \quad \text{--- (2)}$$

Substituting eq (2) in eq (1) and solving for  $I_2(s)$

$$I_2(s) = \frac{10}{1+10s}$$

$$I_2(s) = \frac{1}{s + \frac{1}{10}}$$

Applying Inverse Laplace transform

$$i_2(t) = e^{-t/10}$$

Voltage across capacitor


$$V_c(t) = \frac{1}{C} \int i_2(t) dt$$

$$V_c(t) = \frac{1}{2} \int e^{-t/10} dt$$

$$= \frac{1}{2} \left[ \frac{e^{-t/10}}{-1/10} \right]$$


$$V_c(t) = -5 e^{-t/10}$$

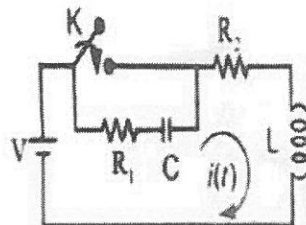9. a) Consider an RLC series circuit as shown figure. Let us assume that the capacitor and inductor are initially uncharged, that is, at  $t=0$ , there is no charge on L or C. Develop an expression for current in the circuit when switch K is closed at  $t = 0$ .






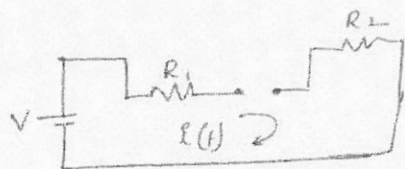9 a At  $t=0^-$ , Capacitor acts as open circuit & Inductor acts as short circuit. & switch is open




$$\text{At } t=0^-, i(t) = 0$$

At  $t=0$ , switch is closed

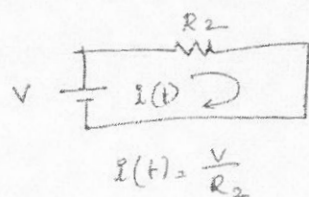

For  $t > 0$

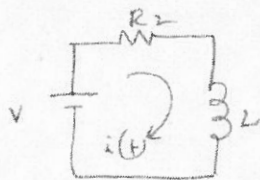

$$V = i(t) R_2 + L \frac{di}{dt}$$

$$\frac{di}{dt} + \frac{R_2}{L} i = \frac{V}{L}$$

It is in the form of 1<sup>st</sup> order non homogeneous Equation

$$\frac{di}{dt} + P i = Q$$

$$i(t) = e^{-Pt} \int Q e^{-Pt} dt + k e^{-Pt}$$

$$\begin{aligned}
 i(t) &= e^{-\frac{R_2}{L}t} \int \frac{V}{L} e^{\frac{R_2}{L}t} + k e^{-\frac{R_2}{L}t} \\
 &= e^{-\frac{R_2}{L}t} \frac{\frac{V}{L} e^{\frac{R_2}{L}t}}{\frac{R_2}{L}} + k e^{-\frac{R_2}{L}t} \\
 i(t) &= \frac{V}{R_2} + k e^{-\frac{R_2}{L}t}
 \end{aligned}$$


At  $t = 0$

$$i(0) = \frac{V}{R_2} + k$$

$$k = 0$$

$$i(t) = \frac{V}{R_2}$$

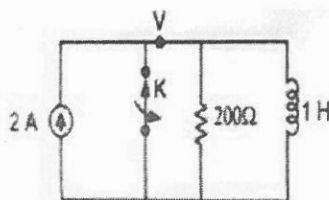- b) For the circuit shown in figure, Analyse the circuit after switch is closed at  $t=0$  and find the transient current for  $t>0$ .



At  $t=0^-$ , the switch is open. The inductor acts as a short circuit in steady state. The current source of 2A is therefore flowing through the inductor.

$$i(0^-) = 2A$$

Since the current through an inductor cannot change instantaneously,

$$i(0^+) = i(0^-) = 2A$$

**Circuit for  $t > 0$ :**

When the switch is closed at  $t = 0$ , the current source is shorted. The circuit is now a simple RL circuit. The inductor will discharge through the  $200\Omega$  resistor.

**Differential Equation:**

Apply KVL around the loop:


$$200i(t) + 1 \frac{di(t)}{dt} = 0$$


$$\frac{di(t)}{dt} + 200i(t) = 0$$

The solution to the differential equation is of the form

$$i(t) = Ae^{-200t} \quad \text{Where } A \text{ is a constant.}$$

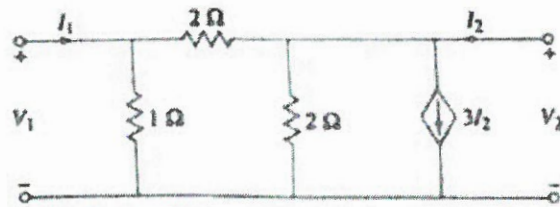10. a) For the network shown in Figure, Find Y parameters.



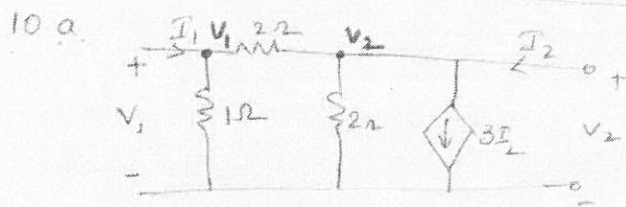

Applying KCL at node 1

$$-I_1 + \frac{V_1}{1} + \frac{V_1 - V_2}{2} = 0$$

$$V_1 \left[ 1 + \frac{1}{2} \right] - \frac{V_2}{2} = I_1$$

$$V_1 \left[ \frac{3}{2} \right] + V_2 \left[ -\frac{1}{2} \right] = I_1 \quad \text{--- (1)}$$

Applying KCL at node 2

$$\frac{V_2 - V_1}{2} + \frac{V_2}{2} + 3I_2 - I_2 = 0$$

$$V_1 \left[ -\frac{1}{2} \right] + V_2 \left[ \frac{1}{2} + \frac{1}{2} \right] = -2I_2$$

$$V_1 \left[ -\frac{1}{2} \right] + V_2 = -2I_2$$

$$V_1 \left[ \frac{1}{4} \right] + V_2 \left[ +\frac{1}{2} \right] = I_2 \quad \text{--- (2)}$$

From eq (1) & (2)

$$I_1 = \frac{3}{2} V_1 - \frac{1}{2} V_2$$

$$I_2 = \frac{1}{4} V_1 + \frac{1}{2} V_2$$

$$\Rightarrow \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} \frac{3}{2} & -\frac{1}{2} \\ \frac{1}{4} & \frac{1}{2} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$\therefore \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} \frac{3}{2} & -\frac{1}{2} \\ \frac{1}{4} & \frac{1}{2} \end{bmatrix}$$

b) Express h parameters in terms of ABCD parameters.

**Hybrid Parameters in Terms of ABCD Parameters** We know that

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

Rewriting the second equation,

$$I_2 = -\frac{1}{D}I_1 + \frac{C}{D}V_2$$

Comparing with

$$I_2 = h_{21}I_1 + h_{22}V_2,$$

$$h_{21} = -\frac{1}{D}$$

$$h_{22} = \frac{C}{D}$$

Also,

$$V_1 = AV_2 - B\left[-\frac{1}{D}I_1 + \frac{C}{D}V_2\right] = \frac{B}{D}I_1 + \left[\frac{AD - BC}{D}\right]V_2$$


Comparing with

$$V_1 = h_{11}I_1 + h_{12}V_2,$$

$$h_{11} = \frac{B}{D}$$

$$h_{12} = \frac{AD - BC}{D} = \frac{\Delta T}{D}$$

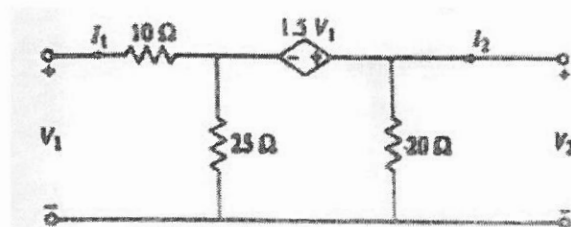11. For the network shown in figure Find Z and T parameters.



11. Z parameters:

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

T parameters:

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

Applying KVL to mesh ①

$$V_1 = 10I_1 + 25I_1 - 25I_3$$

$$\boxed{V_1 = 35I_1 - 25I_3} \quad \text{--- ①}$$

Applying KVL to mesh ②

$$V_2 = 20(I_2 + I_3)$$

$$\boxed{V_2 = 20I_2 + 20I_3} \quad \text{--- ②}$$

Applying KVL to mesh ③

$$25(I_3 - I_1) - 1.5V_1 + 20(I_3 + I_2) = 0$$

$$-25I_1 + 20I_2 + 45I_3 - 1.5V_1 = 0 \quad \text{--- ③}$$

Substituting eq ① in eq ③

$$-25I_1 + 20I_2 + 45I_3 - 1.5[35I_1 - 25I_3] = 0$$

$$-25I_1 + 20I_2 + 45I_3 - 52.5I_1 + 37.5I_3 = 0$$

$$-77.5I_1 + 20I_2 + 82.5I_3 = 0$$

$$I_3 = \frac{77.5I_1 - 20I_2}{82.5}$$

$$\boxed{I_3 = 0.94I_1 - 0.242I_2} \quad \text{--- ④}$$



Substituting eq (4) in eq (1)

$$\begin{aligned} V_1 &= 35 I_1 - 25 [0.94 I_1 - 0.24 I_2] \\ &= 35 I_1 - 23.5 I_1 + 6 I_2 \end{aligned}$$

$$\boxed{V_1 = 11.5 I_1 + 6 I_2} \quad \text{--- (5)}$$

Substituting eq (4) in eq (2)

$$\begin{aligned} V_2 &= 20 I_2 + 20 [0.94 I_1 - 0.24 I_2] \\ &= 20 I_2 + 18.8 I_1 - 4.8 I_2 \end{aligned}$$

$$\boxed{V_2 = 18.8 I_1 + 15.2 I_2} \quad \text{--- (6)}$$

2. Parameters:

from eq (5) & (6)

$$\begin{bmatrix} 11.5 & 6 \\ 18.8 & 15.2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$\therefore \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} 11.5 & 6 \\ 18.8 & 15.2 \end{bmatrix}$$

T parameters:

from eq (6)

$$I_1 = \frac{V_2 - 15.2 I_2}{18.8}$$

$$\boxed{I_1 = 0.053 V_2 - 0.81 I_2} \quad \text{--- (7)}$$

substituting eq (7) in (5)

$$V_1 = 11.5 [0.053 V_2 - 0.81 I_2] + 6 I_2$$

$$V_1 = 0.61 V_2 - 9.32 I_2 + 6 I_2$$

$$\boxed{V_1 = 0.61 V_2 - 3.32 I_2} \quad \text{--- (8)}$$

from eq (7) & (8)

$$\begin{bmatrix} 0.61 & -3.32 \\ 0.053 & -0.81 \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix} = \begin{bmatrix} V_1 \\ I_1 \end{bmatrix}$$

$$\therefore \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 0.61 & -3.32 \\ 0.053 & -0.81 \end{bmatrix}$$